
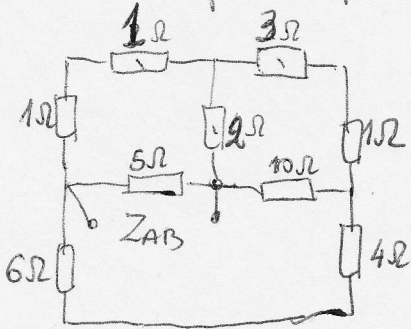


# Zadanie do Kolokwium I (przygotowanie)

1. Calculate input impedance  $Z_{AB}$

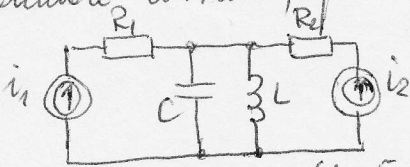



2. Calculate currents, powers & balance of powers in the circuit




$$i_1(t) = 2\sqrt{2} \sin \omega t, \quad i_2(t) = 5 \sin(\omega t + 45^\circ)$$

$$R_1 = 2\Omega, \quad R_2 = 3\Omega, \quad X_L = \omega L = 10\Omega, \quad X_C = \frac{1}{\omega C} = 5\Omega$$

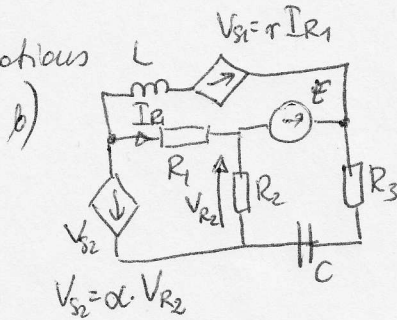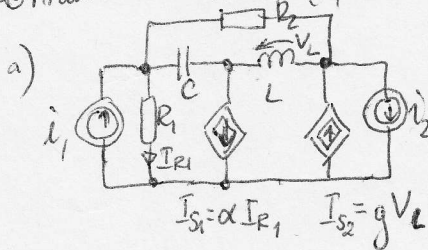3. Formulate nodal (a) & mesh (b) equations



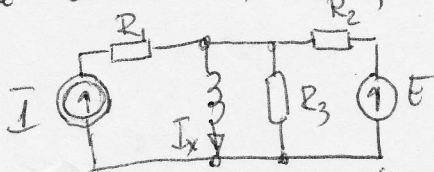
4. Calculate current  $I_x$  using Thevenin theorem



$$i(t) = 10\sqrt{2} \sin \omega t, \quad e(t) = 30 \sin(\omega t - 45^\circ)$$

$$R_1 = 2\Omega, \quad R_2 = 10\Omega, \quad R_3 = 5\Omega, \quad \omega L = 4\Omega$$

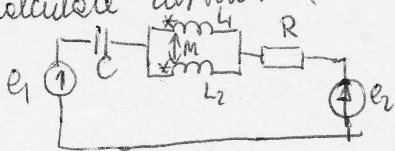
5. Calculate currents & voltages of the coupled inductors



$$e_1 = 20\sqrt{2} \sin(\omega t + 90^\circ), \quad e_2 = 30\sqrt{2} \sin(\omega t - 90^\circ)$$

$$R = 5\Omega, \quad \omega L_1 = 20\Omega, \quad \omega L_2 = 30\Omega, \quad \omega M = 10\Omega, \quad \frac{1}{\omega C} = 10\Omega$$

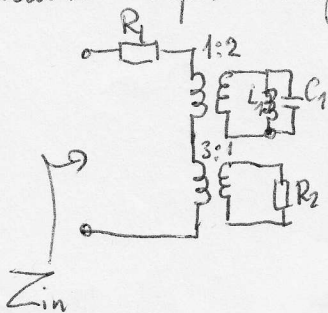6. Calculate input impedance of the circuit



$$R_1 = 10\Omega$$

$$R_2 = 3\Omega$$

$$\omega L_1 = 20\Omega$$

$$\frac{1}{\omega C_1} = 40\Omega$$