

1. Determine the state space description of the circuit

