

Circuits and systems II, Tutorial No 4

1. Transform state-space description into differential equation of n th order

A) $\dot{x} = \begin{bmatrix} -1 & 2 \\ 4 & -5 \end{bmatrix} x + \begin{bmatrix} 7 \\ 9 \end{bmatrix} u$

B) $\dot{x} = \begin{bmatrix} -2 & 1 & 0 \\ -1 & -1 & 2 \\ -3 & 4 & -3 \end{bmatrix} x$

2. Transform one equation of n th order into state space description


a) $\frac{d^2x}{dt^2} + 2\frac{dx}{dt} + 3x = 3e_1$

Hints: $x_1 = x$, $x_2 = \frac{dx_1}{dt}$


b) $\frac{d^3x}{dt^3} + 4\frac{d^2x}{dt^2} + 3\frac{dx}{dt} + 7x = e_1 + 2e_2$

Hints: $x_1 = x$, $x_2 = \frac{dx_1}{dt}$, $x_3 = \frac{dx_2}{dt}$

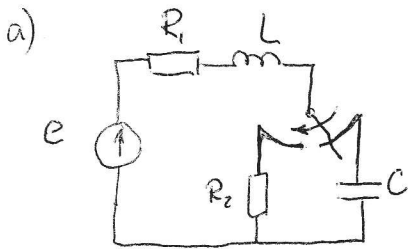
3. Determine $u_c(t)$, $i_L(t)$ in transient state after switching (classical method)



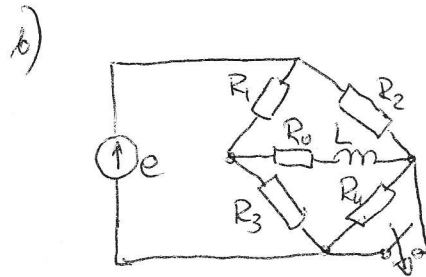
$e(t) = 20 \sin(t + 45^\circ)$
 $R_1 = 1\Omega$, $R_2 = 9\Omega$
 $L = 2H$, $C = 1F$



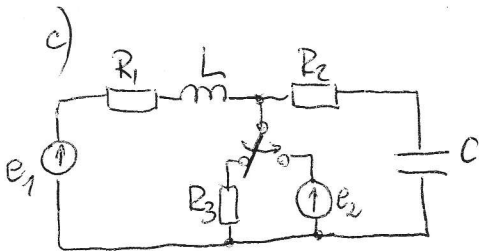$e(t) = 10\sqrt{2} \sin t$
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 10\Omega$, $R_4 = 5\Omega$, $R_5 = 3\Omega$
 $L = 2H$



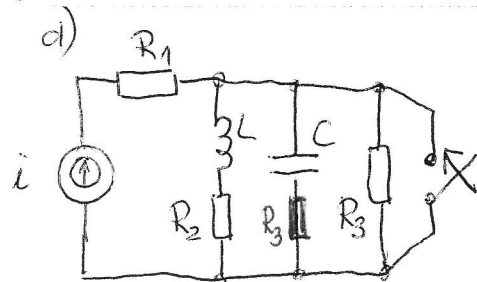$R_1 = 2\Omega$, $R_2 = R_3 = 1\Omega$
 $L = 2H$, $C = 1F$
 $e_1(t) = 20\sqrt{2} \sin t$
 $e_2(t) = 40\sqrt{2} \sin(t + 90^\circ)$



$R_1 = 10\Omega$, $R_2 = 2\Omega$, $R_3 = 4\Omega$
 $L = 1H$, $C = 100\mu F$
 $i(t) = 12A$

4. Calculate inverse Laplace transform of the fraction

a) $F(s) = \frac{s+4}{(s+1)(s+2)}$

b) $F(s) = \frac{3s^2+2s}{s^2+6s+8}$

c) $F(s) = \frac{s+1}{s(s+3)^2}$

d) $F(s) = \frac{2s^2+s+1}{s^2+4s+10}$

e) $F(s) = \frac{3s+7}{s^2+2s+5}$

f) $F(s) = \frac{3s^2+2s+1}{s^2+6s+10}$