
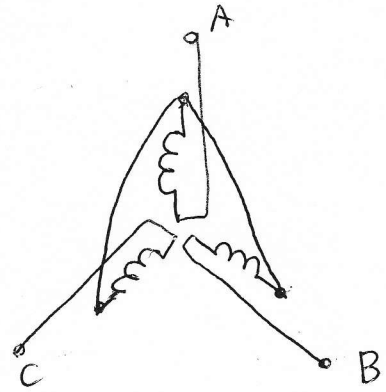
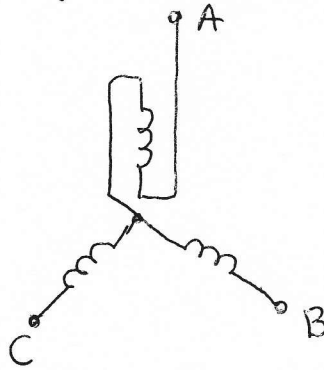


Circuits and systems, No 11

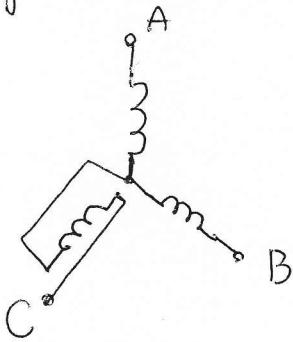1. Construct the symmetrical components of phase voltages of 3-phase generators of the windings connected as below




2. Calculate the symmetrical components of the line voltages


a) $|U_{AB}| = |U_{BC}| = 2000V$
 $|U_{CA}| = 0$

b) $|U_{AB}| = 1000V$
 $|U_{BC}| = 1000V$
 $|U_{CA}| = 800V$

3. Calculate the symmetrical components of currents using Kirchhoff's laws for symmetrical components. Assume symmetrical generator of $|E_{ph}| = 200V$ (a)
 $Z = 10 + j10$

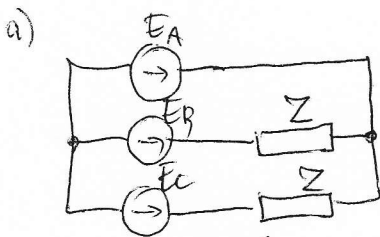


symmetric generator

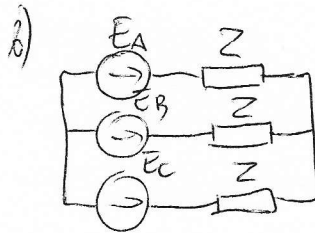

$|E_{ph}| = 300V$


Non-symmetric generator of the structure 1a.

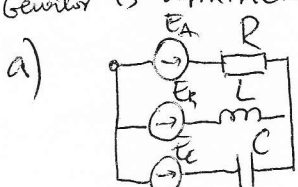4. Calculate symmetrical components of phase currents in the circuit. Generator is symmetric.



$R = X_L = X_C = 10$

$|E_{ph}| = 200$

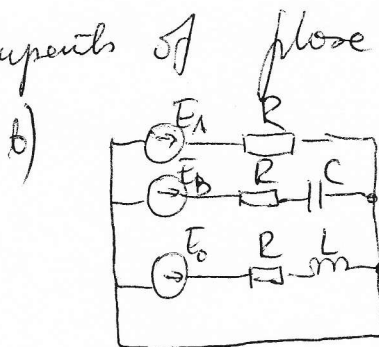

$|E_{ph}| = 600V$

$R = 10\Omega$

$X_L = 10\Omega$

$X_C = 20\Omega$