
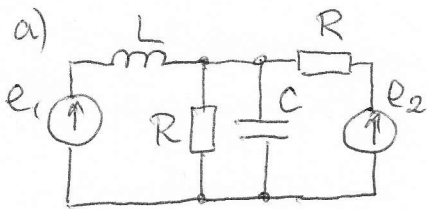


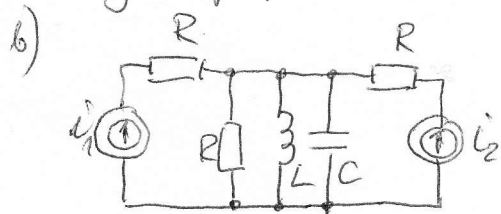1. Calculate currents in the circuit using superposition theorem





$e_1(t) = 20$
 $e_2(t) = 10\sqrt{2} \sin t$
 $L = 5H, C = 0,1F, R = 5\Omega$




$i_1(t) = 5$
 $i_2(t) = 4\sqrt{2} \sin(t + 90^\circ)$
 $L = 2H$
 $C = 0,25F$
 $R = 2\Omega$

2. Eliminate magnetic couplings

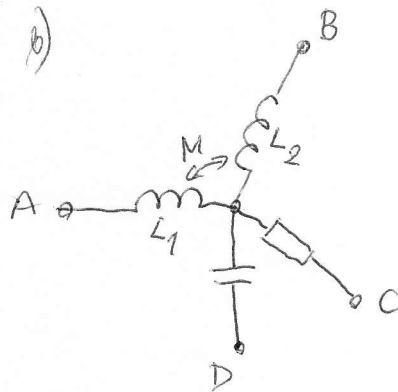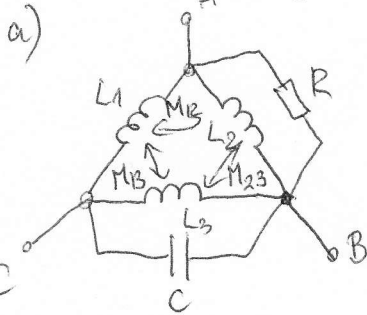


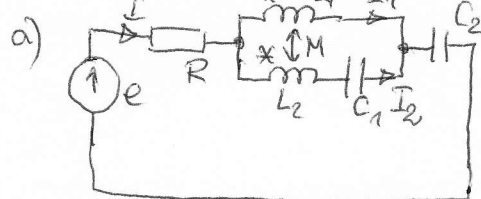3. Calculate currents & voltages on inductances




$e(t) = 20\sqrt{2} \sin(\omega t + 90^\circ)$
 $\omega L_1 = 20\Omega, \omega L_2 = 30\Omega, \omega M = 10\Omega$
 $R = 20, \frac{1}{\omega C_1} = 20\Omega, \frac{1}{\omega C_2} = 30\Omega$

inductances

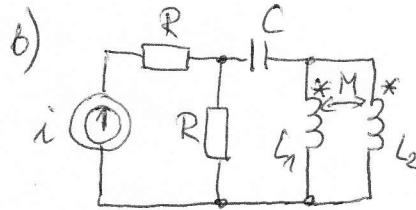


$i(t) = 10\sqrt{2} \sin(t - 90^\circ)$
 $R = 1\Omega, C = 1F$
 $L_1 = 3H, L_2 = 2H, M = 1H$

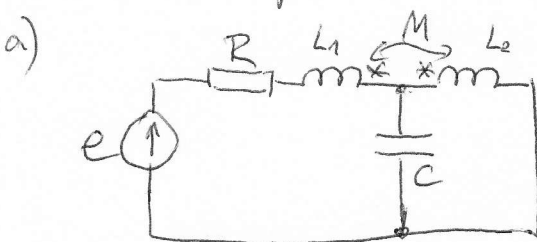4. Calculate powers of elements & balance of powers



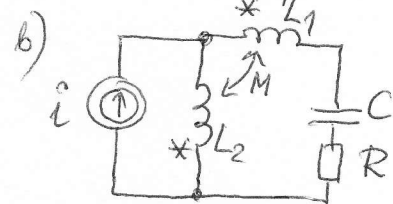$e(t) = 100\sqrt{2} \sin(\omega t + 90^\circ)$
 $\omega L_1 = 50\Omega, \omega L_2 = 60\Omega, \omega M = 20\Omega$
 $R = 80\Omega, \frac{1}{\omega C} = 50\Omega$



$i(t) = 10 \sin(\omega t + 45^\circ)$
 $R = 20\Omega, \frac{1}{\omega C} = 10\Omega$
 $\omega L_1 = 20\Omega, \omega L_2 = 30\Omega, \omega M = 10\Omega$