

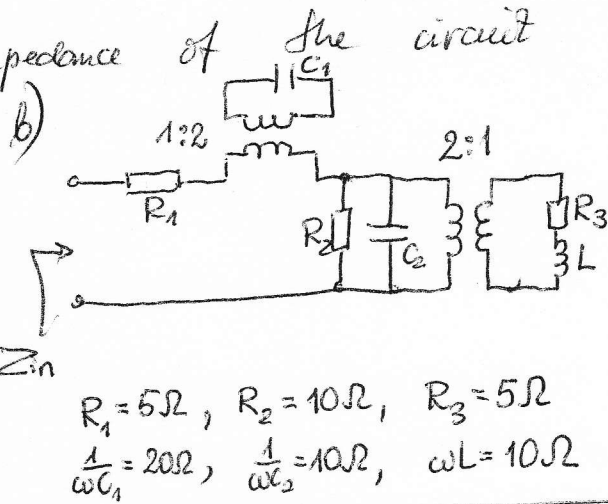
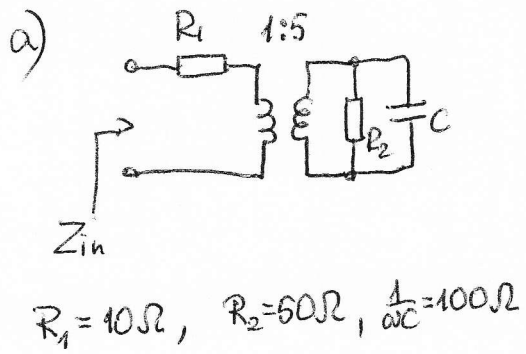


Circuits & systems - tutorials no 7


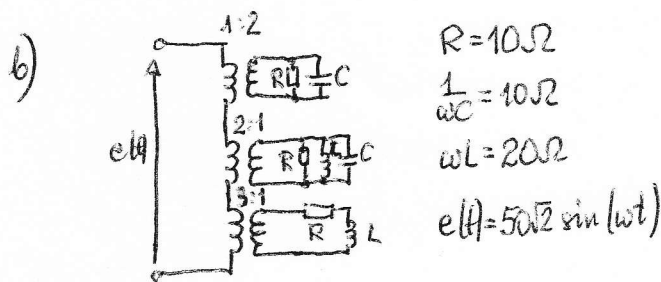
1. Calculate the input impedance of the circuit





2. Calculate currents in the circuit

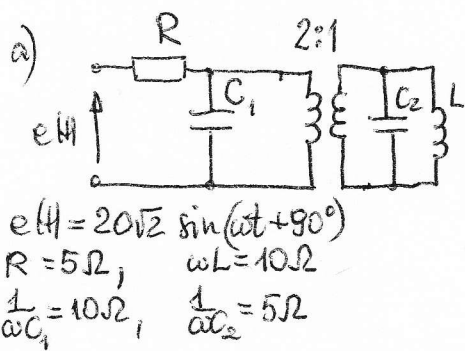

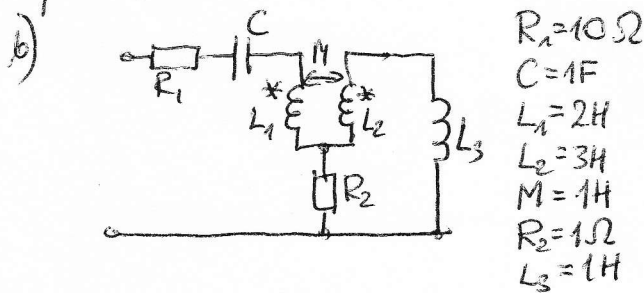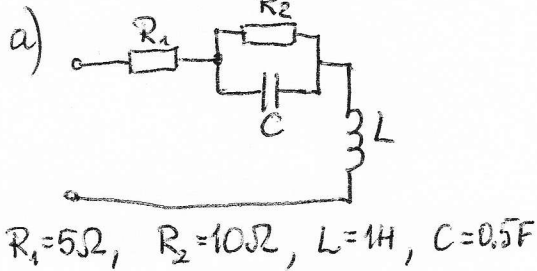3. Determine the resonance frequency of the circuit



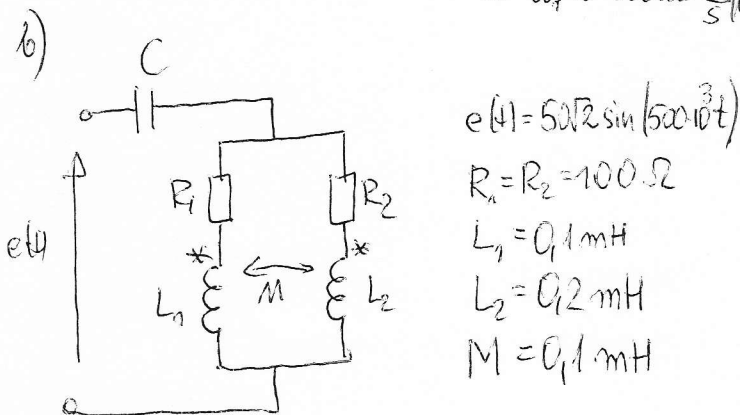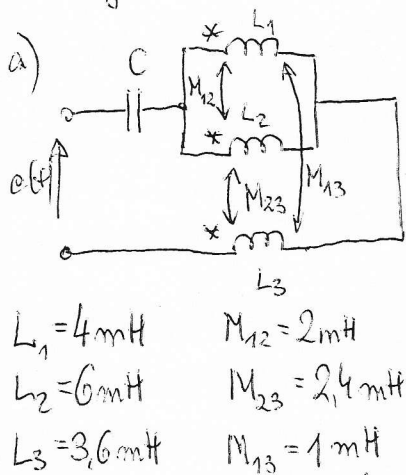4. Adjust value of C in the circuit to get the resonance state at $\omega_1 = 5000 \frac{\text{rad}}{\text{s}}$ (a) at $\omega_1 = \omega = 50000 \frac{\text{rad}}{\text{s}}$ (b)



Calculate currents & voltages of coils if $e(t) = 100\sqrt{2} \sin(\omega_1 t)$
 5000

Calculate currents in the resonant state